

Regulator Prototype


James Eyler

Procedure:

3.3 Volt

$V_{IN} = 2.9$, $I_{IN-MAX} = 0.5$

Circuit

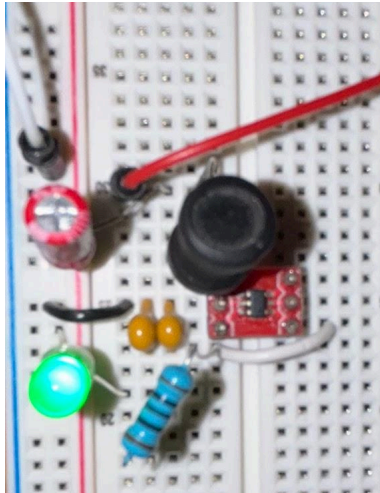

Measurement

Without Electronic Load

$R_{LED} = 100.3 \Omega$

$V_{out} = 3.309 V$

$V_F = 2.619 V$

$I_{LED} = 6.879 mA$

With Electronic Load

$V_{OUT} = 3.30 V \rightarrow$ From DMM

$V_{OUT} = 3.295 V \rightarrow$ From Electronic Load

$I_{OUT} = 30 mA$

$I_{TOTAL} = 30 mA + 6.879 mA = 36.879 mA$

$V_{IN} = 2.90 V$


$I_{IN} = 0.045 A$

$P_{IN} = 2.9 * 0.045 A = 0.1305 W$

$P_{OUT} = 3.30 * 36.879 mA = 0.0123 W$

$Eff = (P_{OUT} / P_{IN}) * 100 = 93\%$


$V_{RPP} = 189.14 mV$

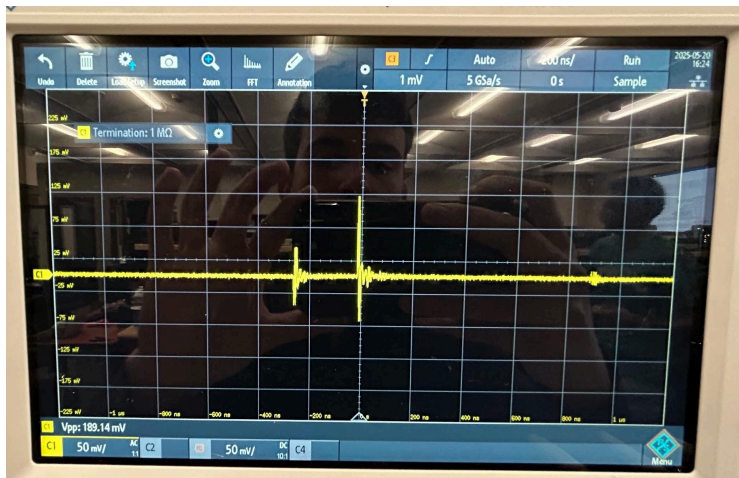

5.0 Volt

$V_{IN} = 2.9$, $I_{IN-MAX} = 0.5$

Circuit

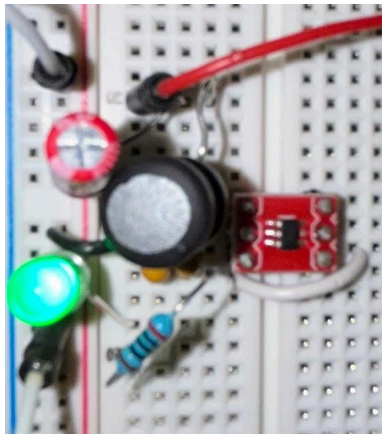

Measurement

Without Electronic Load

$R_{LED} = 199.7 \Omega$

$V_{out} = 5.029 V$

$V_F = 2.77 V$

$I_{LED} = 11.296 mA$

With Electronic Load

$V_{OUT} = 5.0 V \rightarrow$ From DMM

$V_{OUT} = 4.998 V \rightarrow$ From Electronic Load

$I_{OUT} = 23 mA$

$I_{TOTAL} = 11.296 mA + 23 mA = 34.296 mA$

$V_{IN} = 2.90 V$


$I_{IN} = 0.063 A$

$$P_{IN} = 2.9 \text{ V} \cdot 0.063 \text{ A} = 0.1725 \text{ W}$$

$$P_{OUT} = 5.0 \text{ V} \cdot 34.296 \text{ mA} = 0.172 \text{ W}$$

$$\text{Eff} = (P_{OUT} / P_{IN}) \cdot 100 = 94\%$$

$$V_{RPP} = 197.47 \text{ mV}$$

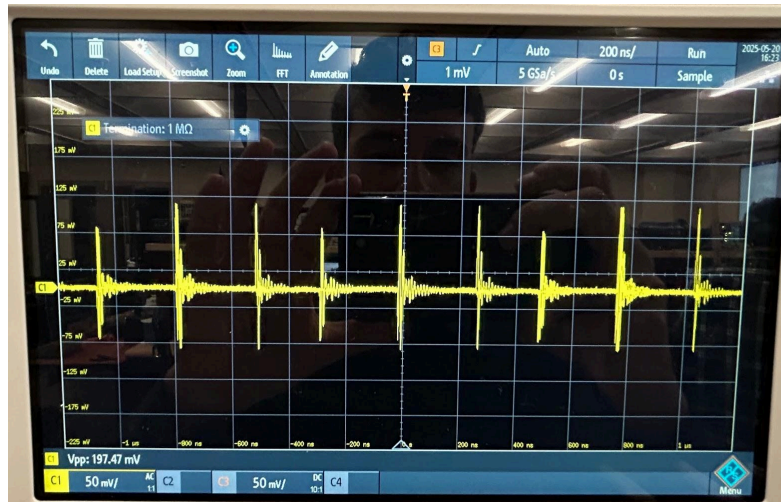

7.0

The results in procedure 4 and 5 were as expected with the regulator based on the datasheets of the regulator chips as well as the data from the WEBENCH tool. All of the values also match components that were used in the circuit such as resistance values and the Turn on voltage for the DIODE.

What I learned - I learned a lot about using the chip, keeping in mind things such as wire length (because this can affect the functionality of the circuit), as well as using the oscillator tool to measure values that are as small as the ripple voltage of the output. I also learned how to use a thermal camera, showing that there is a range that is shown by the camera that has the values shown in the image as well as the ability to see a specific spot using the center crosshair.